

Introduction to Quantum Programming and Semantics

Lecture 11: Classical quantum circuits

Chris Heunen



University of Edinburgh

Overview










- CNOT circuits
- Bennett's trick
- Phase-free ZX diagrams

dictionary Circuits





ZX-diagrams

e.g.:

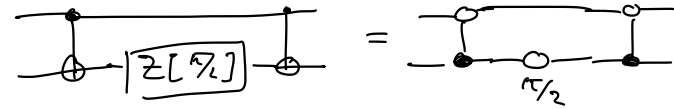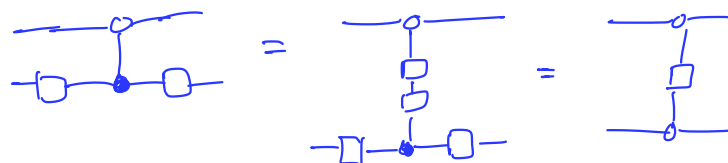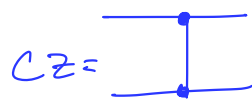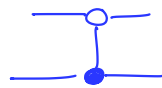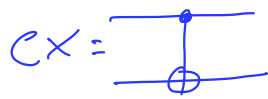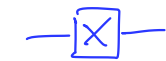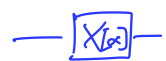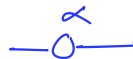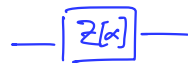

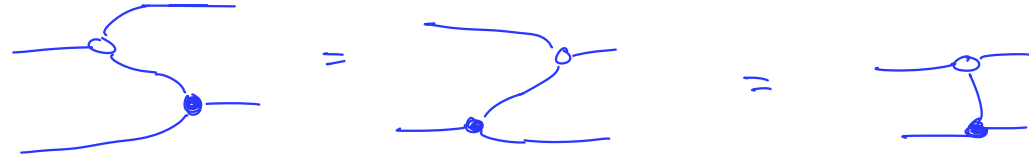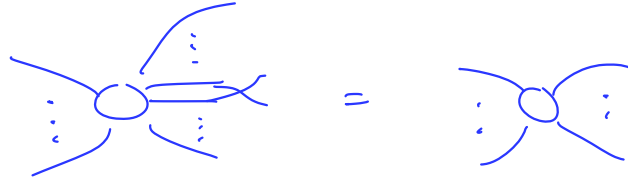$\mathbb{Z}_X$ diagrams have extreme 'only connectivity matters':



2x calculus is tool to reason about circuits. Solve problems like:

- synthesis: given high-level description of computation/unitary,
find circuit that implements it

- optimisation: given a circuit C that implements U ,
find a smaller C' that also implements U

- (classical) simulation: given C that implements U , (not given quantum computer)
and an input $|\psi\rangle$,
- compute measurement probabilities for $U|\psi\rangle$ (strong)
- sample measurement outcome for $U|\psi\rangle$ (weak)

CNOT circuits

Parity

any CNOT circuit is a phase-free ZX diagram



what about converse?


def: a function of form $f(x_1, \dots, x_n) = x_{i_1} \oplus \dots \oplus x_{i_n}$ is called a parity map

can think about linear algebra over $\mathbb{F}_2 = \{0, 1\}$, $x \cdot y = x \text{ AND } y$
 $x + y = x \text{ XOR } y$

e.g. $(1 \ 0 \ 1) \begin{pmatrix} a \\ b \\ c \\ d \end{pmatrix} = a \oplus c \oplus d$

$$\underbrace{\begin{pmatrix} 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 \end{pmatrix}}_{\text{parity matrix}} \begin{pmatrix} a \\ b \\ c \\ d \end{pmatrix} = \begin{pmatrix} a \oplus c \oplus d \\ b \oplus c \\ a \oplus d \\ d \end{pmatrix}$$

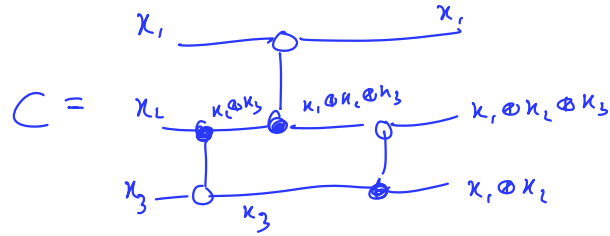Parity matrix : can turn CNOT circuit into parity matrix,



$$C|x_1, x_L, x_3\rangle = |x_1, x_1 \oplus x_L \oplus x_3, x_1 \oplus x_L\rangle$$

$$\begin{pmatrix} 1 & 0 & 0 \\ 1 & 1 & 1 \\ 1 & 1 & 0 \end{pmatrix} \begin{pmatrix} x_1 \\ x_L \\ x_3 \end{pmatrix} = \begin{pmatrix} x_1 \\ x_1 \oplus x_L \oplus x_3 \\ x_1 \oplus x_L \end{pmatrix}$$

more generally:



gives parity matrix

$$\begin{pmatrix} \vdots & & \\ & \ddots & \\ & & 1 \\ & & & \ddots & \\ & & & & 1 \end{pmatrix} \leftarrow j$$

$= E^{ij}$ elementary matrix

$$E^{ij} A = A' \leftarrow \text{row } i' = \text{row } j + \text{row } i$$

$$A E^{ij} = A' \leftarrow \text{col } j' = \text{col } j + \text{col } i$$

CNOT circuit synthesis

- start with a parity matrix P , empty circuit C
- do Gauss-Jordan reduction on columns of P
 - whenever E^{ij} applied, append CNOT^{ji} to C
- repeat until eliminated P

C implements P

Bennett's trick

Reversible computing

where do circuits come from?

one source: classical computations

$$f: \{0,1\}^n \rightarrow \{0,1\}^k \quad \rightsquigarrow$$

$$f: \{0,1\}^n \rightarrow \{0,1\} \quad \rightsquigarrow \text{Bennett's trick}$$

e.g.: $\text{NOT}: \{0,1\} \rightarrow \{0,1\} \quad \rightsquigarrow$

$$\text{CNOT}: \{0,1\}^2 \rightarrow \{0,1\}^2 \quad \rightsquigarrow$$

$$(\mathbb{C}^2)^{\otimes n} \xrightarrow{U_f} (\mathbb{C}^2)^{\otimes n}$$

$$|x\rangle \mapsto |f(x)\rangle$$

$$(\mathbb{C}^2)^{\otimes n+1} \xrightarrow{U_f} (\mathbb{C}^2)^{\otimes n+1}$$

$$|x, y\rangle \mapsto |x, f(x) \oplus y\rangle$$

$$X: \begin{array}{l} |0\rangle \mapsto |1\rangle \\ |1\rangle \mapsto |0\rangle \end{array}$$


$$\text{CX}: |x, y\rangle \mapsto |x, x \oplus y\rangle$$

$$= |x, x \oplus y\rangle$$



Phase-free ZX diagrams

Parity normal form

parity matrix

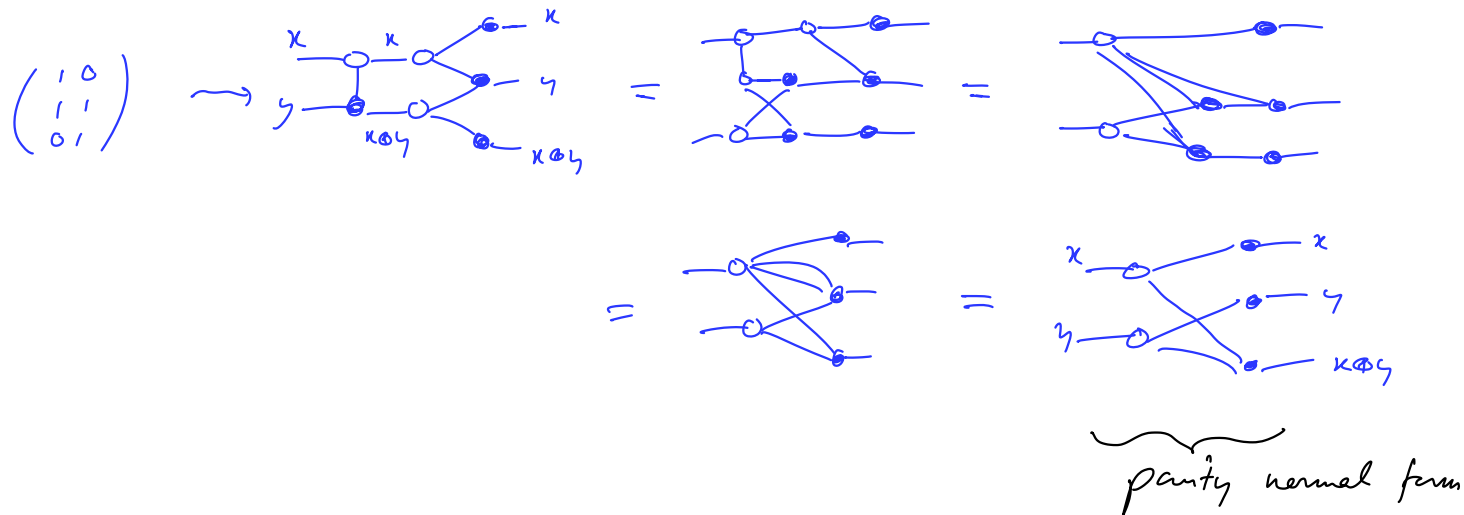

Reduction to parity form

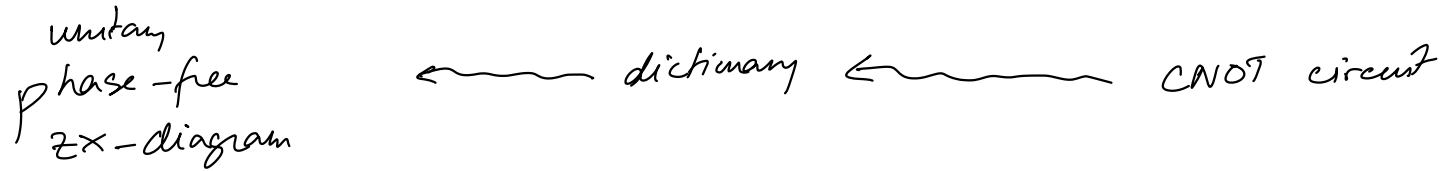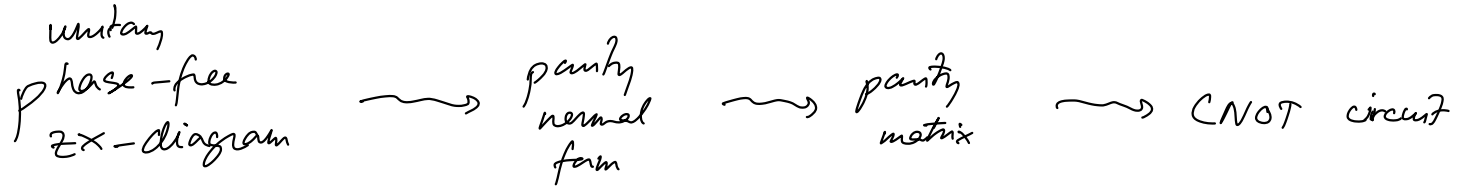

Summary:

- ZX diagrams are (complexity-theoretically) hard to rewrite algorithmically
- Special class of CNOT diagrams easier, comes down to parity checking
- Bennett's trick makes classical functions reversible, useful for oracles
- Special class of phase-free ZX diagrams easier