

# Introduction to Quantum Programming and Semantics

## Lecture 14: Circuit optimisation

Chris Heunen



University of Edinburgh


# Overview

- Universal quantum circuits
- Phase polynomials
- Phase gadgets
- Circuit optimisation

# Phase polynomials
 
# Phase polynomials

(arbitrary)  
 What happens if we add phases to CNOT/Clifford circuits



$$Z[\alpha]: |k\rangle \mapsto e^{i\alpha \cdot k} |k\rangle$$

$$|kyz\rangle \xrightarrow{1} |k, y\oplus z, z\rangle$$

$$\xrightarrow{2} e^{i\alpha(y\oplus z)} |k, y\oplus z, z\rangle$$

$$\xrightarrow{3} e^{i\alpha(y\oplus z)} |k, x\oplus y\oplus z, z\rangle$$

$$\xrightarrow{4} e^{i\alpha(y\oplus z)} |k, x\oplus y\oplus z, x\oplus y\rangle$$

$$\xrightarrow{5} e^{i(\alpha(y\oplus z) + \beta(x\oplus y))} |k, x\oplus y\oplus z, x\oplus y\rangle$$

$\mapsto \dots$

$$\mapsto e^{i[\alpha(y\oplus z) + \beta(x\oplus y) + \gamma(y\oplus z) + \theta\gamma]} |k, y\oplus z, z\rangle$$

"phase polynomial"




any CNOT+phase circuit describes  
 a unitary of the form

$$U = |k\rangle \mapsto e^{i\theta(\vec{k})} |L\vec{k}\rangle$$

phase polynomial
parity matrix

# Phase gadgets

# Phase gadgets

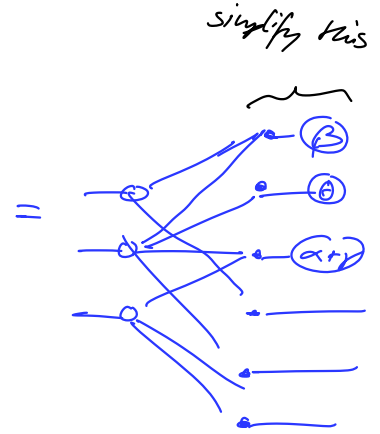  

1-legs:


$$\text{---} \alpha : |k\rangle \mapsto \begin{cases} 1 & \text{if } k=0 \\ e^{i\alpha} & \text{if } k=1 \end{cases} = e^{i\alpha \cdot k}$$

k-legs:

$$\text{---} \alpha : |x_1 \dots x_k\rangle \mapsto e^{i\alpha(x_1 \oplus \dots \oplus x_k)}$$

phase gadget

as a diagonal unitary:

 


$$: |x_1 \dots x_k\rangle \mapsto e^{i\alpha(x_1 \dots x_k)} |x_1 \dots x_k\rangle$$


# Phase gadgets

can fuse!


rule:

 

e.g.:

 

=

 

algorithm for CNOT + phase optimisation:



1. unfuse all phases and treat as outputs
2. compute parity normal form of phase-free part
3. perform gadget-fusion
4. extract CNOT + phase circuit.

(there are several choices for step 4.)

# Circuit optimisation




# CNOT ladders

  


- Naive extraction:
1. unfuse a phase gadget + replace using Cor
  2. repeat until can't
  3. synthesise CNOT circuit from phase-free diagram

# CNOT ladders

*Lots of wasted gates*

 


vs

 

# CNOT ladders

better extraction strategy:

 1. find "extended biadjacency matrix"
2. identify  $k$  lin. indep. rows
3. reduce each row
4. "extract" phases and repeat



gadgets

$$\begin{pmatrix} 1 & 1 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \\ \dots & \dots & \dots \\ 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{pmatrix}$$

outputs

add col 1  
to col 2

$$\begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \\ \dots & \dots & \dots \\ 1 & 1 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{pmatrix}$$

add col 3  
to col 2

$$\begin{pmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ \dots & \dots & \dots \\ 1 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 1 \end{pmatrix}$$

pro: - good at low Clifford depth  
- better with ancillas

con: CNOT depth inconsistent

# Summary:

- ZX diagrams with  $\pi/4$  phases fully universal but difficult
- Phase polynomials/gadgets bring structure
- Can be used to rewrite circuits