

Introduction to Quantum Programming and Semantics

Lecture 11: Classical quantum circuits

Chris Heunen



University of Edinburgh

Overview






- CNOT circuits
- Bennett's trick
- Phase-free ZX diagrams

dictionary

circuit





ZX-diagram

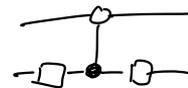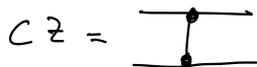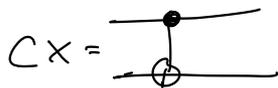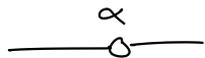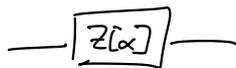

ZX-diagrams

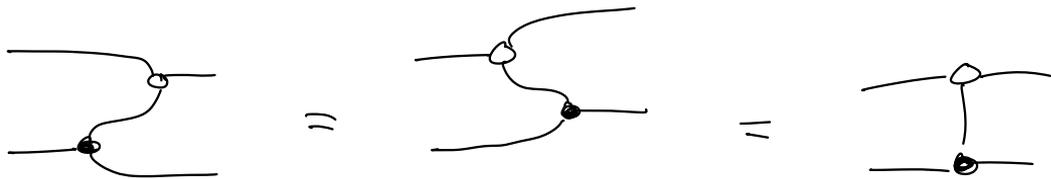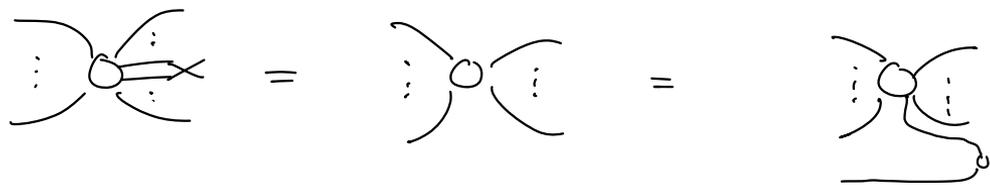ZX diagrams have extreme 'only connectivity matters':



ZX calculus is a tool to reason about quantum circuits. Solve problems like:

- synthesis: given a high-level description of a computation/unitary, find a circuit that implements it
- optimisation: given a circuit C that implements U , find a 'smaller' C' that also implements U .
- (classical) simulation: given C that implements U , and an input $|\psi\rangle$,
 - compute measurement probabilities for $U|\psi\rangle$ ("strong")
 - sample measurement outcome for $U|\psi\rangle$ ("weak")(not given quantum hardware)

CNOT circuits

Parity

any CNOT circuit induces a phase-free ZX-diagram



what about converse?

def: a function of form $f(x_1, \dots, x_n) = x_{i_1} \oplus \dots \oplus x_{i_n}$ is called "parity function"


can think about this as linear algebra over $\mathbb{F}_2 = \{0, 1\}$, $x \cdot y = x \text{ AND } y$
 $x + y = x \text{ XOR } y$

e.g. $(1 \ 0 \ 1 \ 1) \begin{pmatrix} a \\ b \\ c \\ d \end{pmatrix} = a \oplus c \oplus d$

$\underbrace{\begin{pmatrix} 1 & 0 & 1 & 1 \\ 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 \end{pmatrix}}_{\text{"parity matrix"}} \begin{pmatrix} a \\ b \\ c \\ d \end{pmatrix} = \begin{pmatrix} a \oplus c \oplus d \\ b \oplus c \\ a \oplus d \\ d \end{pmatrix}$

can turn CNOT into parity matrix:


Parity matrix

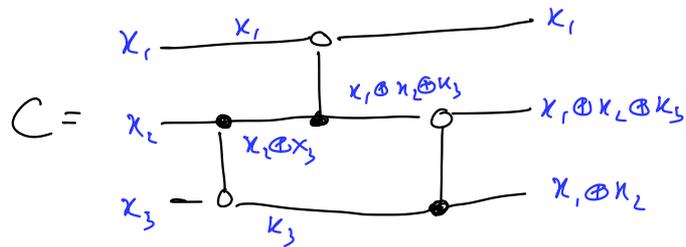

$$C |x_1, x_2, x_3\rangle = |x_1, x_1 \oplus x_2 \oplus x_3, x_1 \oplus x_2\rangle$$

$$\begin{pmatrix} 1 & 0 & 0 \\ 1 & 1 & 1 \\ 1 & 1 & 0 \end{pmatrix} \begin{pmatrix} x_1 \\ x_2 \\ x_3 \end{pmatrix} = \begin{pmatrix} x_1 \\ x_1 \oplus x_2 \oplus x_3 \\ x_1 \oplus x_2 \end{pmatrix}$$

more generally:

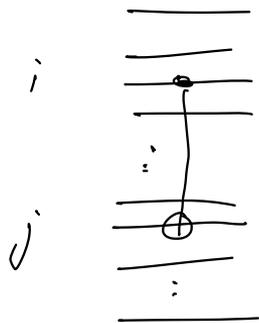

gives parity matrix

$$E^{ij} = \begin{pmatrix} 1 & & & & \\ & \ddots & & & \\ & & 1 & & \\ & & & \ddots & \\ 0 & & & & 1 \end{pmatrix}$$

elementary matrix operation

CNOT circuit synthesis

- start with a parity matrix P , empty circuit C
- do Gauss-Jordan elimination on columns of P
whenever apply E^{ij} , append CNOT to C
swap two rows, use \hookrightarrow with control i target j
- repeat until P eliminated

then C implements P



Bennett's trick

Reversible computing

Where do circuits come from?

one source: classical computations

$$f: \{0,1\}^n \longrightarrow \{0,1\}^n \quad \rightsquigarrow$$

$$f: \{0,1\}^n \longrightarrow \{0,1\} \quad \rightsquigarrow$$

Bennett's
trick

$$(\mathbb{C}^2)^{\otimes n} \xrightarrow{U_f} (\mathbb{C}^2)^{\otimes n}$$

$$|x\rangle \longmapsto |f(x)\rangle$$

$$(\mathbb{C}^2)^{\otimes n+1} \xrightarrow{U_f} (\mathbb{C}^2)^{\otimes n+1}$$

$$|x, y\rangle \longmapsto |x, y \oplus f(x)\rangle$$

e.g. NOT : $\{0,1\} \longleftrightarrow \{0,1\}$ \rightsquigarrow

$$X : \begin{array}{l} |0\rangle \longmapsto |1\rangle \\ |1\rangle \longmapsto |0\rangle \end{array}$$


CNOT : $\{0,1\}^2 \longrightarrow \{0,1\}^2$ \rightsquigarrow

$$CX : |x, y\rangle \longmapsto |x, x \oplus y\rangle$$


Phase-free ZX diagrams

Parity normal form

parity matrix

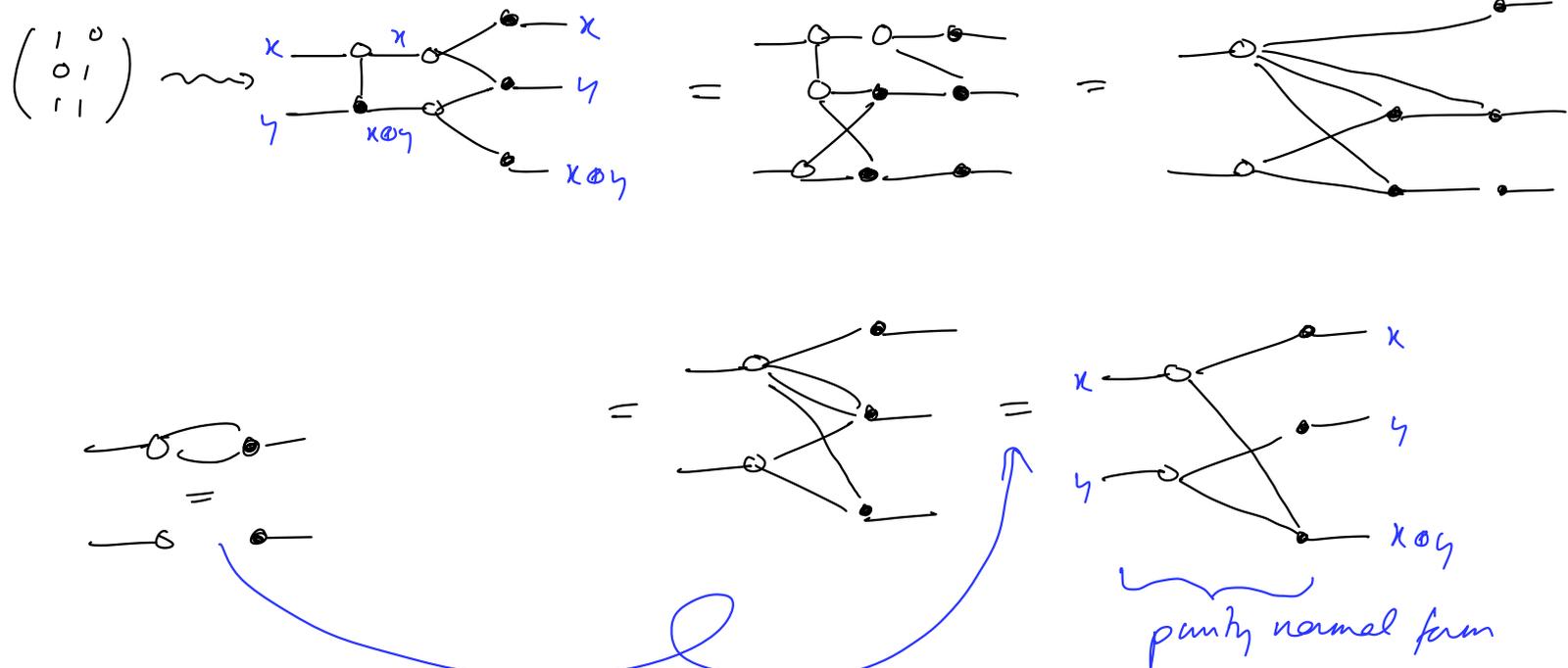

Reduction to parity form

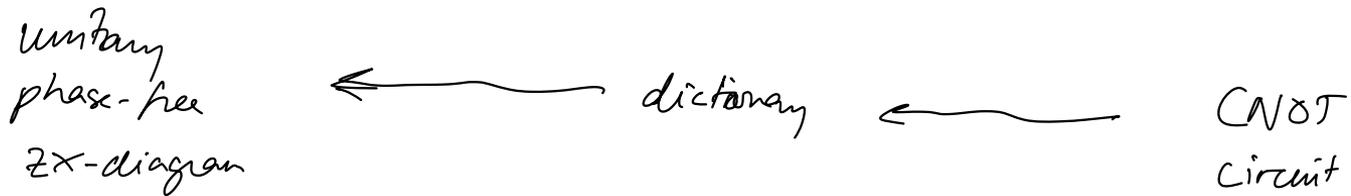

Summary:

- ZX diagrams are (complexity-theoretically) hard to rewrite algorithmically
- Special class of CNOT diagrams easier, comes down to parity checking
- Bennett's trick makes classical functions reversible, useful for oracles
- Special class of phase-free ZX diagrams easier